

6.13 $i = C \frac{dV}{dt}$ or $V(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = V(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau$

\therefore for $t \in [0, 2\text{ms}]$, $V(t) = \frac{1}{5\mu} \int_0^t \frac{15}{2} \tau d\tau = \underline{7.5 \text{E}5 t^2 \text{ (in V)}}$

at $t = 2\text{ms}$, $V(2\text{ms}) = 3\text{V}$

for $t \in [2\text{ms}, 4\text{ms}]$ $V(t) = V(2\text{ms}) + \frac{15\text{m}}{5\mu} (t - 2\text{ms}) = \underline{3 + 3\text{E}3 (t - 2\text{ms})}$

at $t = 4\text{ms}$, $V(4\text{ms}) = 9\text{V}$

for $t \in [4\text{ms}, 6\text{ms}]$ $V(t) = V(4\text{ms}) - \frac{5\text{m}}{5\mu} (t - 4\text{ms}) = \underline{9 - 1\text{E}3 (t - 4\text{ms})}$

at $t = 6\text{ms}$, $V(6\text{ms}) = 7\text{V}$

for $t \in [6\text{ms}, 8\text{ms}]$ $V(t) = V(6\text{ms}) + \frac{1}{5\mu} \left[\frac{5\text{m}}{2\text{m}} \frac{(t - 6\text{ms})^2}{2} - 5\text{m} (t - 6\text{ms}) \right]$
 $= 7 + \frac{1}{4} \text{E}6 (t - 6\text{ms})^2 - 1\text{E}3 (t - 6\text{ms})$

at $t = 8$, $V(8) = 6\text{V}$

The energy stored in the capacitor is $\frac{1}{2} CV^2$, so

At $t = 1.4\text{ms}$, $V(1.4\text{ms}) = 1.47 \Rightarrow E = \frac{1}{2} 5\mu \cdot 1.47^2 = \underline{5.4\mu\text{J}}$


$t = 3.3\text{ms}$, $V(3.3\text{ms}) = 6.9 \Rightarrow E = \underline{119\mu\text{J}}$

$t = 4.3\text{ms}$, $V(4.3\text{ms}) = 8.7 \Rightarrow E = \underline{189\mu\text{J}}$

$t = 6.7\text{ms}$, $V(6.7\text{ms}) = 6.42 \Rightarrow E = \underline{103\mu\text{J}}$

$t = 8.5\text{ms}$, $V(8.5\text{ms}) = 6 \Rightarrow E = \underline{90\mu\text{J}}$

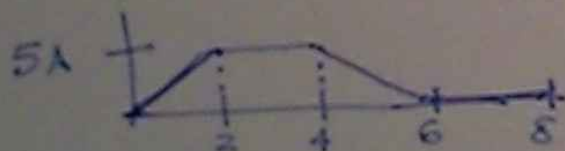6.27 $V(t) = L \frac{di}{dt}$ or $i = \frac{1}{L} \int V \Rightarrow$ the graph for $i(t)$ is




To find the peak, we note that the slope is $\frac{V}{L} = \frac{5}{2}$ so
 $\frac{1}{2} \int_0^2 5 dt = 5\text{ (A)}$

6.47

$$V_c = \frac{15}{15+10} \cdot 25 = 15(V) \Rightarrow E_c = \frac{1}{2} C V^2 = \frac{1}{2} \cdot 5 \times 10^{-3} \cdot 15^2 = 0.56 J$$


$$I_L = \frac{25(V)}{(10+15)(\Omega)} = 1(A) \Rightarrow E_L = \frac{1}{2} L I^2 = \frac{1}{2} \cdot 0.5 \cdot 1^2 = 0.25 J$$

6.55

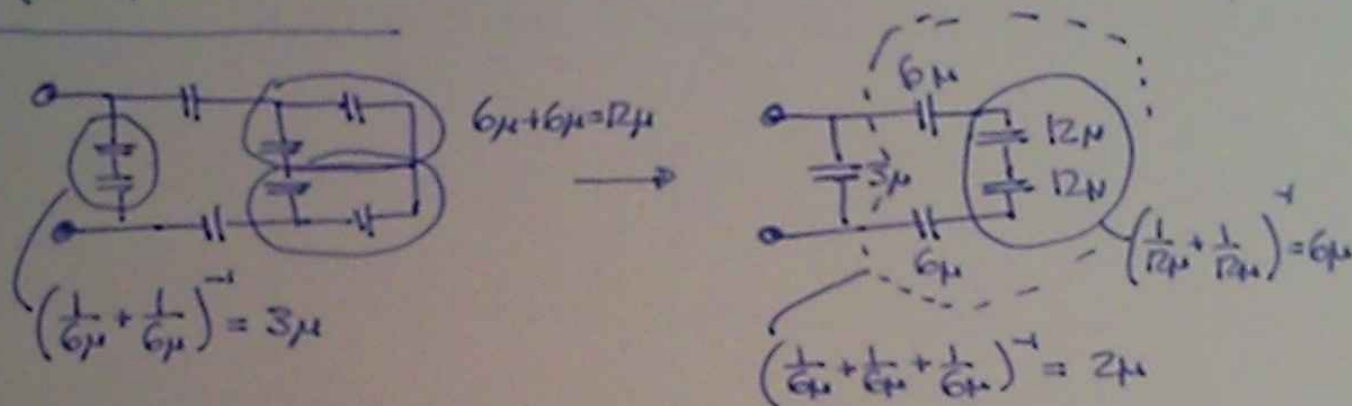

$$\Rightarrow C_{eff} = 3\mu + 2\mu = 5\mu F$$

6.56

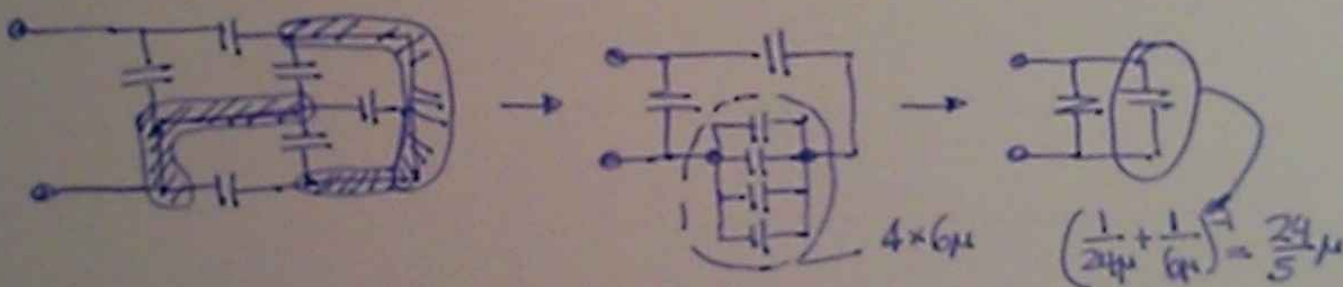

$$\Rightarrow C_{eff} = \frac{24}{5}\mu + 6\mu = \frac{54}{5}\mu F$$

7.46

The step-by-step method for discontinuous variables (i.e. other than capacitor voltages and inductor currents) can be described as follows

I. Solve for V_c (or I_L) \Rightarrow Replace Cap (or Ind.) by a voltage (or current) source $V_c(t)$ (or $I_L(t)$) and solve the resulting circuit.


II. 1) Find $V_c(0^-)$ (or $I_L(0^-)$) with the $t < 0$ -circuit.

2) Set $V_c(0^+) = V_c(0^-)$ (or $I_L(0^+) = I_L(0^-)$) and substitute the capacitor with a voltage source $V_c(0^+)$ (or the inductor with a current source $I_L(0^+)$).

- 3) Compute the initial condition for the variable of interest, say x , such that $x(0^+) = \text{value for the } t > 0 \text{ circuit}$ (with the caps replaced by voltage sources).
- 4) Compute $x(\infty)$ for the $t > 0$ circuit.
- 5) Compute R_{TH} as seen by the capacitor (or inductor) for the $t > 0$ circuit.
- 6) $x(t) = x(\infty) + [x(0) - x(\infty)] e^{-t/\tau}$; $\tau = R_{TH}C$ (or R_{TH}/L).


For our problem,

1) $t < 0$

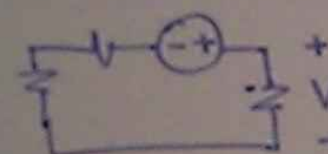


$$V_o = \frac{2k}{6k} 12 = 4V$$

2) $t > 0$

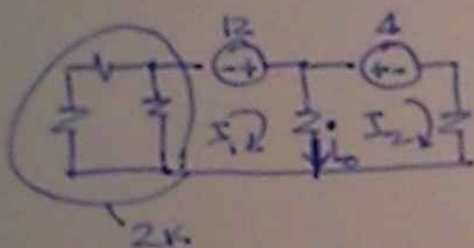


$$\begin{aligned} I_1 \cdot 2k - 12 + 2k(I_1 - I_2) &= 0 \\ 4 + 2kI_2 + 2k(I_2 - I_1) &= 0 \\ \Rightarrow I_1 &= \frac{10}{3} \text{ mA}, \quad I_2 = \frac{4}{6} \text{ mA} \\ \Rightarrow \underline{i_o(0^+) = I_1 - I_2 = \frac{8}{3} \text{ mA}} \end{aligned}$$

3) $t > 0$

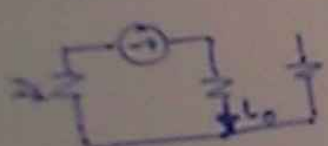

$$\Rightarrow i_o(\infty) = \frac{12}{4k} = 3 \text{ mA}$$

5) $t > 0$

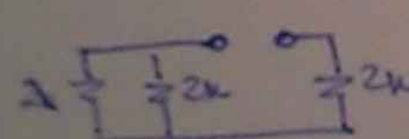


$$\Rightarrow R_{TH} = \left(\frac{1}{2k} + \frac{1}{2k} \right)^{-1} + 2k = 3k \Omega$$

6) $i(t) = 3 \text{ mA} + \left(\frac{8}{3} \text{ mA} - 3 \text{ mA} \right) e^{-t/0.6} \text{ (A)}$

where $0.6 \text{ ms} = \tau = R_{TH} \cdot C = 3k \cdot 200\mu = 600 \text{ ms}$


7.47
=

$t < 0$

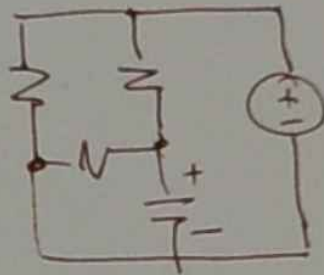

$$V_C(0) = \frac{(12)(6k)}{6k + 6k} = 6V$$

$t > 0$

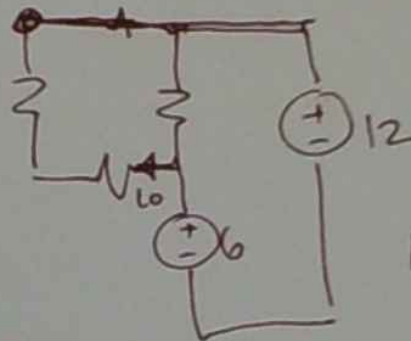


$$I_o(0) = -\frac{(12-6)}{6k + 6k}$$

$$= -\frac{1}{2} \text{ mA}$$

$t > 0 \quad I_o(\infty) = 0$
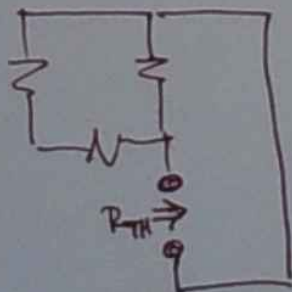
$$\Rightarrow I_o(t) = \frac{1}{2} \text{ mA} e^{-t/\tau} \quad T = R_{TH}C = 200 \text{ ms} = 0.2 \text{ s}$$



$$R_{TH} = 6k \parallel (6k + 6k) = 4k$$

$$C = 50 \mu \Rightarrow \tau = 200 \text{ ms}$$